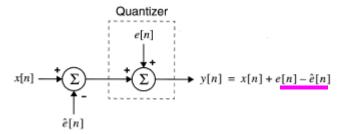
## **Basic Theory of Operation**


In <u>Nyquist rate</u> converters, the error is **reduced** by using a large number of small steps in the quantizer characteristic.

In <u>oversampled data converters</u>, specifically sigma-delta modulators, the error is **corrected** by estimating the error in advance and subtracting it from the input.




However, since the error is not known until it is made, e[n] is not known when  $\hat{e}[n]$  is needed. Therefore, some means must be found to estimate the error.

In the case of **sigma-delta** converters, the error can be estimated by exploiting some knowledge of the frequency domain behavior of the input signal. Specifically, *it is assumed that the signal is changing very slowly from sample to sample*, or equivalently, its bandwidth is much less than the sampling rate. For exceedingly slow signals, a **first-order estimate of the error** to be committed in quantization can be formed. The first-order estimate of the current error e[n] is *simply* the previous error e[n-1].

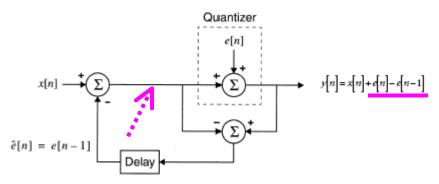

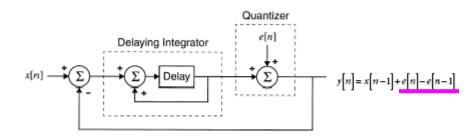With a few straightforward steps, the system can be transformed into that of Fig below, where the delay element is now immersed in an integrator feedback loop.



Fattaruso, J.W., Williams III, L.A. "Oversampled Analog-to-Digital and Digital-to-Analog Converters" *The VLSI Handbook.* Ed. Wai-Kai Chen Boca Raton: CRC Press LLC, 2000


## DSM topológia variációk

#### Zajformálás (zaj-differenciálás) és szűrés spektrum szeparálás


LP (Low Pass) MOD1:

Visszacsatolással (tracking loop) átlagosan zérus értékű az (ábrán diszkrét-idejű) integráló kimenete, ez minimalizálja a kisfrekvenciás differenciát x és c között.

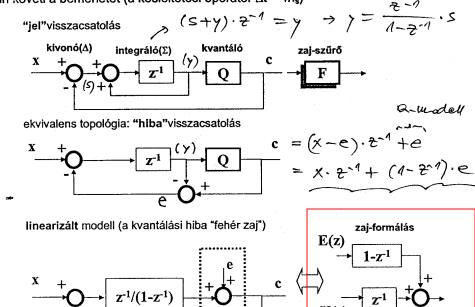
Tehát a nagy mintagyakoriságú numerikus mintasorozat (c: data stream) lokális "átlag"értéke pontosan követi a bemenetet (a késleltetési operátor ∆t = 1/fs)



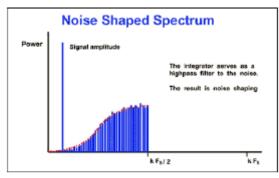A <u>jel</u> és <u>kvantálási-zaj</u> spektrum <u>szeparálódik</u> (!), a keskenysávú *jelre* a transzfer függvény:  $z^{-1}$  (ez csak késleltetés), míg a szélessávú *zajt formáló* transzfer függvény: 1 -  $z^{-1}$  (ez diszkrét idejű **elsőrendű** differenciáló  $\rightarrow$  frekvencia szelektív: nagyfrekvenciás kiemelő, felüláteresztő szűrő)



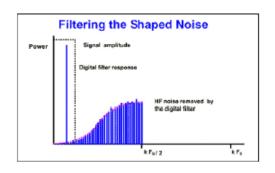Affect of the integrator in the sigmadelta modulator




C(z)

X(z)

jel-késleltetés


## LP MOD1:

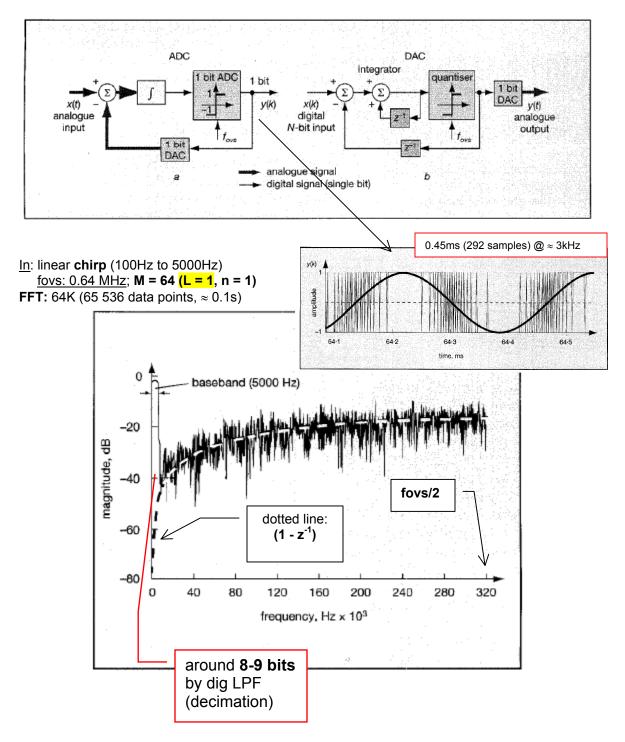

A second-order estimate of e[n] may be formed by assuming that the error e[n] varies <u>linearly</u> with time. In this case, an *estimate* of the current error e[n] may be computed by changing the previous error e[n-1] by an amount equal to the change between e[n-2] and e[n-1]. The second order *error* estimate is thus


$$\hat{e}[n] = e[n-1] + (e[n-1] - e[n-2]) = 2e[n-1] - e[n-2]$$

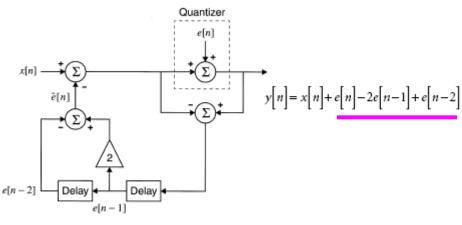and the second-order modulator is the following




Second-order error estimation.

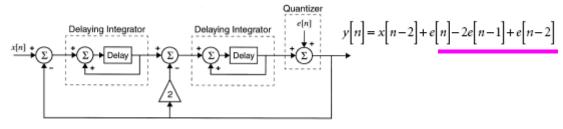After a number of steps, that the modulator can be transformed into a modulator in which the feedback loop delays are again immersed in practical *integrator* blocks



Second-order equivalent modulator.

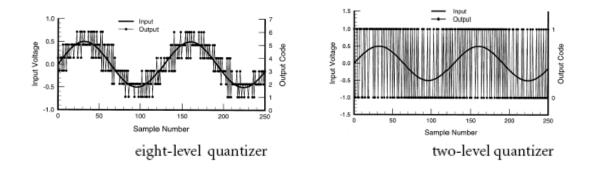Fig's show the simulated output of the modulator when fed with a simple sinusoidal input



Fattaruso, J.W., Williams III, L.A. "Oversampled Analog-to-Digital and Digital-to-Analog Converters" *The VLSI Handbook.* Ed. Wai-Kai Chen Boca Raton: CRC Press LLC, 2000

## PCM vs. 2<sup>nd</sup> order DSM

#### Uniform Quantizer:

48-Msample/s input sequence, consisting of a 48-kHz sinusoid with small amplitude [plus a small amount of white noise such that the input signal-to-noise ratio (SNR) is 100 dB]. Fig. 2(a) shows the power <u>spectral</u> <u>density (PSD) plot</u> of the resulting quantizer output sequence, and Fig. 2(b) shows a <u>time-domain plot</u> of the quantizer output sequence over two periods of the sinusoid

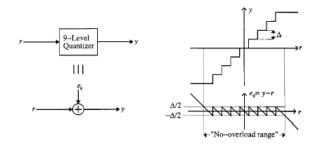


Fig. 1. Ideal nine-level uniform quantizer.

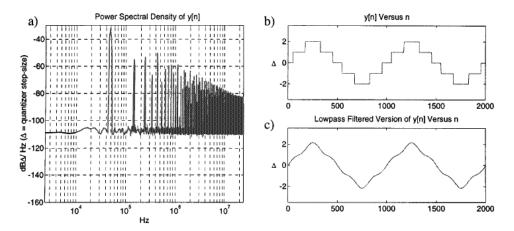


Fig. 2. (a) PSD plot of the quantizer output in decibels, relative to the quantization step-size, per hertz. (b) Time-domain plot of the quantizer output. (c) Time-domain plot of the quantizer output filtered by a sharp lowpass filter with a cutoff frequency of 500 kHz.

### $\Delta \Sigma$ Modulator:

Same 48-Msample/s input sequence considered above is applied to the input of the modulator, and the discrete-time integrators in the modulator are clocked at 48 MHz. Fig. 4(a) shows the <u>PSD plot</u> of the resulting modulator output sequence, , and Fig. 4(b) shows a <u>time-domain plot</u> of over two periods of the sinusoid



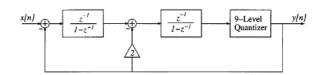



Fig. 3. Second-order  $\Sigma\Delta$  modulator architecture.

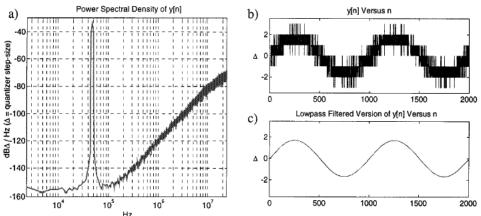

 


Two important **differences** with respect to the uniform quantization example shown in Fig. 2 are apparent: (1) the quantization noise PSD is significantly **attenuated** at low frequencies, and (2) **no** spurious tones are visible anywhere in the discrete-time spectrum.

## <u>LP MOD2</u>:

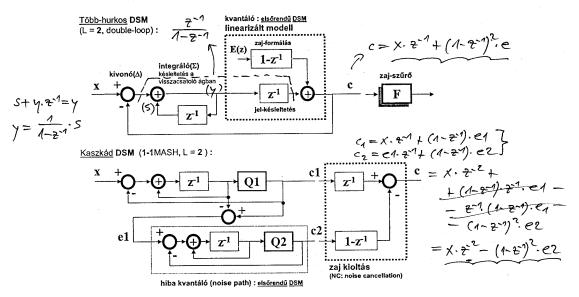

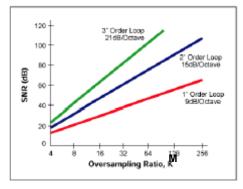2.3 A linearizált kvantáló modellt felhasználva, igazoljuk, hogy másodrendű (L = 2) zajformáló az alábbi *több-hurkos* (multi-loop) illetve kaszkád (MASH) átalakító alapváltozat

A kaszkád DSM kimenete mindig multi-bites (még akkor is, ha a kvantálók 1 bitesek), miért?




Relationship between order of sigma-delta modulator and the amount of oversampling necessary to achieve a particular SNR

#### ANALOG MULTIBIT <u>LP</u> <u>MOD1</u>

#### 2.6 Multi-bites (n > 1), analóg DSM.

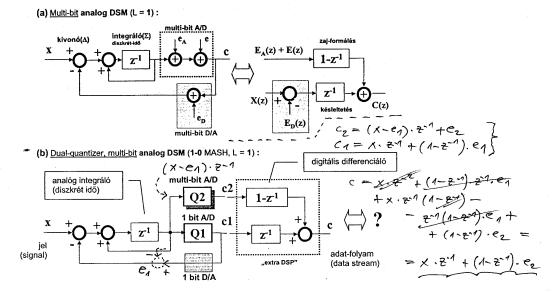
(a) Igazoljuk az ekvivalens topológiát (L = 1): a visszacsatoló ágban lévő D/A átalakitó  $e_D$  torzítására nincs zajformálás (a hasznos sávba eső zajt csak a túlmintavételezés csökkenti)! Ezért igen nagy linearitású (kis transzfer torzítású) D/A átalakítót kell használni.

Ráadásul, csak egy órajelnyi késleltetés lehet a hurokban (loop rate = 1 clock latency), ami igen gyors (egy lépéses: word-at-a-time = flash) A/D átalakítót kíván. A modell számba veszi az A/D realizálási hibáját is: plusz e<sub>A</sub> torzítás



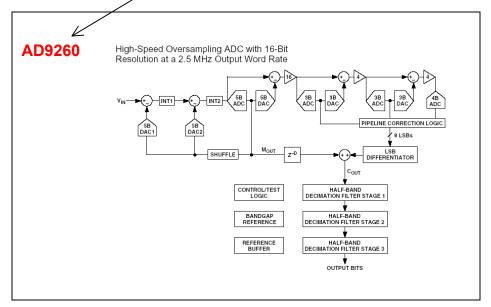
(b) Egy <u>trükk</u> a probléma megoldására: 1-0 MASH két kvantálós architektúra [T. Leslie, B. Singh 1990]; a hatásos kvantáló (Q2) felbontása és a visszacsatolás (Q1) felbontása szétválik ("multibites" kvantálás kontra "1 bites" visszacsatolás). Adjuk meg az ekvivalens topológiát (linearizált kvantáló modellek, hibamentes 1 bites D/A).

A multi-bites A/D a hurkon kívül van, így kell külső szűrő (a hiba korrekcióhoz); de pl. *több* lépéses, párhuzamos műveletvégzésű is lehet a konverter bit-kereső algoritmusa (pipelining), amelynek terjedési késleltetése kompenzálható. (A módszer kombinálja az OSADC és a Nyquist-rate technikákat, lásd 8. példa.)




#### DIGITAL <u>LP MOD1</u> and <u>MOD2</u>

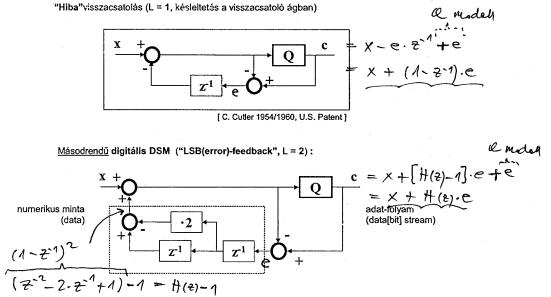2.9 A DSM eljárás egyik alapforrása a *"hiba"visszacsatolás* topológia (self-dithering, deterministic dither). *Analóg* DSM esetén *nem* praktikus az elrendezés, mert a visszacsatoló ágban végzett művelet hibájára nincs zajformálás (lásd 2.6 feladat). Ez nem hátrány digitális DSM esetén (sőt, pl. egyszerű szóhossz csonkítással realizálható a kvantálás és hiba-képzés, lásd 31. oldal)



Ha L > 1 az igény zajformálásra, a késleltetést "predikciós" szűrő helyettesíti (amelynek átvitele: H(z) - 1, ahol H(z) a kívánt zaj-formáló transzfer függvény).

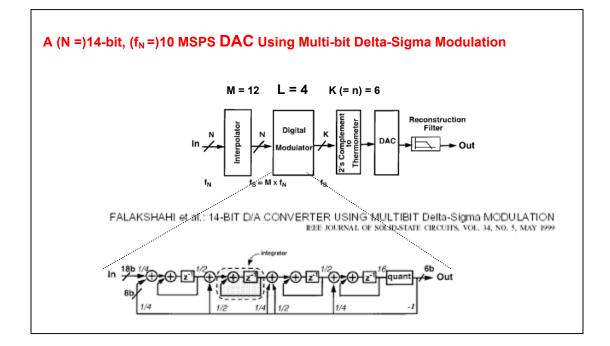Igazoljuk, hogy a vázolt topológia másodrendű zajformáló. Megjegyzés: a szorzás (·2) = shift.




١

A Low-Voltage Low-Power Sigma-Delta Modulator for Broadband Analog-to-Digital Conversion KIYoung Nam, Student Menter, IEEE, Sang-Min Lee, Student Menter, IEEE, David K. Su, Senter Member, IEEE, and Brice A. Wooley, Rillow, IEEE
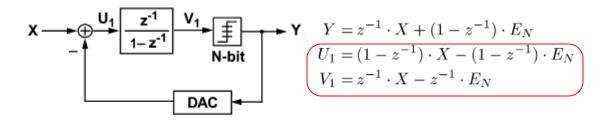
# a feedforward architecture


The input and output of the integrator,  $U_1$  and  $V_1$ , each have a component that depends on the modulator input:



Conventional first-order  $\Sigma\Delta$  modulator.

This *input dependence results in* large signals for  $U_1$  and  $V_1$  when the input is large ( $\rightarrow op \ amp$  clipping, harmonic distortion ...)

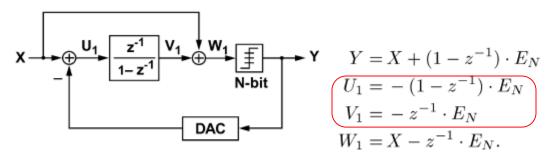The **input-feedforward path** in modulator is a method of relaxing the requirements on analog blocks:



First-order reduced integrator swing range (RISR)  $\Sigma\Delta$  modulator.

The input and output of the integrator,  $U_1$  and  $V_1$  *no longer depend* on the modulator input X. The removal of the input signal component *reduces* the swing at the internal nodes of the modulator which relaxes the headroom requirements, and allows for more efficient *op amp* architectures to be used.

[However, the input-feedforward path presents a couple of *complications*, namely the increased loading the input has to drive, the analog adder at the quantizer input ...]

The approach can be expanded to a second-order noise-differencing modulator:

