Edited by Bill Travis

## The best of design ideas

## Combine two 8-bit outputs to make one 16-bit DAC

Ideas

Steve Woodward, Chapel Hill, NC

NEXPENSIVE, 16-BIT, monolithic DACs can serve almost all applications. However, some applications require unconventional approaches. This Design Idea design concerns circuitry I recently designed for a tunable-diode laser spectrometer for a Mars-exploration application. The control circuitry included two 16-bit DACs that interface to the radiation-hardened, 8051-variant 69RH051A microcontroller. Because of the intended space-flight-qualified specification, everything in the design had to consist solely of components from the NPSL (NASA parts-selection list). This restriction posed a challenge, because, at design finalization, the NPSL included no appropriate, flight-qualified, 16-bit DACs, and the budget included no funds for certification of new devices. I escaped from this impasse by exploiting two fortuitous facts: The update rate of the two DACs was only tens of hertz, and the 69RH-051A had a number of uncommitted, 8bit, 14.5-kHz PWM outputs. These outputs made one 16-bit DAC; a second pair of PWM bits and an identical circuit made the other (**Figure 1**).

Hex inverter IC<sub>1</sub>'s  $V_{CC}$  rail connects to a precision 5V reference. The inverter's



Combine two 8-bit outputs to make one 16-bit DAC .. 85 LED driver provides software-controlled intensity ...... 86 Improve roll-off of Sallen-Key filter ...... 88 AC-coupling instrumentation amplifier improves rejection range of differential dc input voltage.. 88 Simplify computer-aided engineering with scientific-to-engineering conversion .....94 1.5V battery powers white-LED driver ...... 96 Simple V<sub>COM</sub> adjustment uses any logic-supply voltage .. 96 Publish your Design Idea in EDN. See the What's Up section at www.edn.com.

outputs are accurate analog square waves. The low-order PWM-signal output, PWM0, of the 8051 controls the V<sub>3</sub> square wave, and the high-order PWM output, PWM1, controls the V<sub>1</sub> square wave. R2 and R6 passively sum the two square waves in the ratio  $R_2/R_6 = 3290/1$ million=1/255 to produce V, duplicating the 28 ratio of the 16-bit sum. This action makes the dc component of V<sub>4</sub> equal to 5V(REF)(PWM0+255PWM1)/256. Thus, if you write the 0 to 255, high-order byte of a 0 to 65,535, 16-bit DAC setting to the CEX1 register of the 8051 and write the 0 to 255, low-order byte to CEX0, a corresponding 16-bit analog representation appears in the dc component of  $V_4$ . The accuracy of the  $R_2$ -to- $R_6$ ratio is the only limit on the monotonicity and accuracy of this circuit. For example, one part in 25,500=14.5 bits for 1%-tolerance R, and R, and a full 16 bits for 0.3% tolerance or better. But the story doesn't end there. Two problems remain.

The first problem is the extraction of  $V_4$ 's desired dc component from all—or



at least 15 or 16 bits=99.995%-of the undesired square-wave ac ripple. The R<sub>2</sub>- $C_{o}$  lowpass filter does some of this work. If you make C<sub>o</sub> large enough, in principle, the filter could do the whole job. The reason this simple approach wouldn't work is that, to get such a large ripple attenuation of approximately 90 dB with a single-stage RC filter would require an approximately 300-msec time constant and a resultant 3-sec, 16-bit settling time. This glacial response time would be too slow even for this undemanding application. To speed things, the  $R_4$ ,  $R_5$ ,  $R_7$ ,  $C_8$ network synthesizes and then sums V<sub>2</sub>: an inverse-polarity duplicate of V's 14.5kHz ac component. This summation actively nulls out approximately 99% of the ripple. This nullifying action leaves such a small residue that an approximately 2-msec and, therefore, approximately 25-msec-settling-time  $R_3C_9$  product easily erases it.

**The other problem** is compensation for the low, but still nonzero, on-resistance of the HC14 internal CMOS switches, so that the resistance doesn't perturb the critical  $R_2$ -to- $R_6$  ratio. This issue is of no particular concern for  $R_6$ , because the  $R_6$ to-on-resistance ratio is greater than 10,000-to-1, making any associated error negligible. This situation is not the case for  $R_2$ , however, in which, despite the triple-parallel gates, the  $R_2$ -to-on-resistance ratio is approximately 300-to-1, which is small enough to merit attention. Load-cancellation resistor R<sub>1</sub> provides such attention. R<sub>1</sub> sums a current into the R, driving node that, because it is equal in magnitude but opposite in phase to the current through R<sub>e</sub>, effectively cancels the load on the R, drivers. This process makes the combined on-resistance approximately 100 times less important than it otherwise would be. The result is a simple, highly linear and accurate voltageoutput DAC with a respectable, if not blazingly fast, settling time of approximately 25 msec. And the most important result, in this case, was a parts list with an impeccable NPSL-compliant pedigree.□

## LED driver provides software-controlled intensity

Neda Shahi and Bjorn Starmark, Maxim Integrated Products, Sunnyvale, CA

ecent advances in operating efficiency have expanded the use of LEDs from one of mere indicators to becoming driving forces in electronic lighting. Increased reliability and ruggedness (versus other lighting technologies) gives the LED a bright future indeed. Vendors in recent years have introduced many ICs for driving LEDs, but the problem of driving serial chains of LEDs has received less attention. One approach to that problem adapts a bias-supply IC for APDs (avalanche photodiodes) to provide

adjustable-current, software shutdown, and logic

indication of open-circuit faults (**Figure** 1). This design reconfigures the APD-bias IC, IC<sub>1</sub>, to allow its low-voltage DAC output to modulate the high-voltage, current-sense feedback via a high-voltage-output transconductance stage comprising  $Q_2$  and  $Q_3$ . These two complementary transistors provide first-order temperature-compensation sufficient for the application.

Equations from the MAX1932 data



The APD driver, IC,, provides high-voltage LED modules with software-adjustable intensity control.

sheet help you select components for the step-up dc/dc converter. The current-ad-justment transfer function is:

$$I_{OUT} = \frac{V_{CL} - \frac{CODE \times 1.25V}{256} \times \frac{R_2}{R_4}}{R_1},$$

where  $V_{CL}$  is the current-limit threshold (2V), CODE is the digital code to the DAC in decimal format, and  $I_{OUT}$  is the desired output current. For this circuit,

these conditions correspond to a fullscale output of 39 mA and a resolution of 150  $\mu$ A. The three-wire serial interface that controls IC<sub>1</sub> allows you to shut down IC<sub>1</sub> by writing code 00hex to the DAC. The circuit also provides an output-voltage limit. If an LED fails open, the R<sub>5</sub>-R<sub>7</sub> divider limits the output voltage, in this case, to 50V. Simultaneously, the CL pin goes high to indicate the open-fault condition.